

Verilog - Operators

- ▶ Verilog operators operate on several data types to produce an output
- ▶ Not all Verilog operators are synthesizable (can produce gates)
- ▶ Some operators are similar to those in the C language
- ▶ Remember, you are making gates, not an algorithm (in most cases)

Verilog - Operators

Arithmetic Operators

- ▶ There are two types of operators: binary and unary
- ▶ Binary operators:
 - ▶ add(+), subtract(-), multiply(*), divide(/), power(**), modulus(%)

```
//suppose that: a = 4'b0011;  
//              b = 4'b0100;  
//              d = 6; e = 4; f = 2;  
//then,  
a + b //add a and b; evaluates to 4'b0111  
b - a //subtract a from b; evaluates to 4'b0001  
a * b //multiply a and b; evaluates to 4'b1100  
d / e //divide d by e, evaluates to 4'b0001. Truncates fractional part  
e ** f //raises e to the power f, evaluates to 4'b1111  
      //power operator is most likely not synthesizable
```

If any operand bit has a value "x", the result of the expression is all "x".
If an operand is not fully known the result cannot be either.

Verilog - Operators

Arithmetic Operators (cont.)

Modulus operator yields the remainder from division of two numbers

It works like the modulus operator in C

Modulus is synthesizable

```
3 % 2; //evaluates to 1
16 % 4; //evaluates to 0
-7 % 2; //evaluates to -1, takes sign of first operand
7 % -2; //evaluates to 1, takes sign of first operand
```

Verilog - Operators

Arithmetic Operators (cont.)

- ▶ Unary operators
 - ▶ Operators "+" and "-" can act as unary operators
 - ▶ They indicate the sign of an operand

```
i.e., -4 // negative four  
      +5 // positive five
```

!!! Negative numbers are represented as 2's complement numbers !!!

!!! Use negative numbers only as type integer or real !!!

!!! Avoid the use of <sss>'<base><number >in expressions !!!

!!! These are converted to unsigned 2's complement numbers !!!

!!! This yields unexpected results in simulation and synthesis !!!

Verilog - Operators

Arithmetic Operators (cont.)

- ▶ The logic gate realization depends on several variables
 - ▶ coding style
 - ▶ synthesis tool used
 - ▶ synthesis constraints (more later on this)
- ▶ So, when we say "+", is it a...
 - ▶ ripple-carry adder
 - ▶ look-ahead-carry adder (how many bits of lookahead to be used?)
 - ▶ carry-save adder

When writing RTL code, keep in mind what will eventually be needed
Continually thinking about structure, timing, size, power


Verilog - Operators

Arithmetic Operators (cont.)

16-bit adder with loose constraints:

```
set_max_delay 2 [get_ports sum*]
```

max delay = 0.8ns, area = 472 = 85 gates

 


Verilog - Operators

Arithmetic Operators (cont.)

16-bit adder with tighter constraints:

```
set_max_delay 0.5 [get_ports sum*]
```

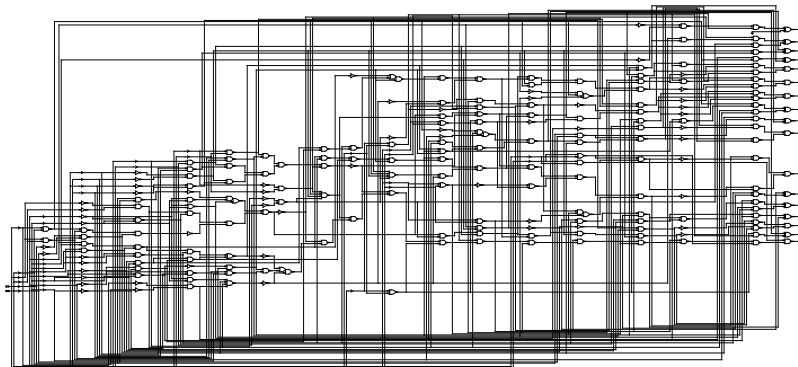max delay = 0.5ns, area = 2038 = 368gates



Verilog - Operators

Logical Operators

- ▶ Verilog Logical Operators
 - ▶ logical-and(&&) //binary operator
 - ▶ logical-or(||) //binary operator
 - ▶ logical-not(!) //unary operator

//suppose that: a = 3 and b = 0, then...

(a && b) //evaluates to zero

(b || a) //evaluates to one

(!a) //evaluates to 0

(!b) //evaluates to 1

//with unknowns: a = 2'b0x; b = 2'b10;

(a && b) // evaluates to x

//with expressions...

(a == 2) && (b == 3) //evaluates to 1 only if both comparisons are true

Verilog - Operators

Logical Operators (.cont)

- ▶ Logical operators evaluate to a 1 bit value
 - ▶ 0 (false), 1 (true), or x (ambiguous)
- ▶ Operands not equal to zero are equivalent to one
- ▶ Logical operators take variables or expressions as operators

Verilog - Operators

Relational Operators (.cont)

- ▶ greater-than ($>$)
- ▶ less-than ($<$)
- ▶ greater-than-or-equal-to ($>=$)
- ▶ less-than-or-equal-to ($<=$)

Relational operators return logical 1 if expression is true, 0 if false

```
//let a = 4, b = 3, and...  
//x = 4'b1010, y = 4'b1101, z = 4'b1xxx  
a <= b //evaluates to logical zero  
a > b //evaluates to logical one  
y >= x //evaluates to logical 1  
y < z //evaluates to x
```


!!! Note: These are expensive and slow operators at gate level !!!

Verilog - Operators

Equality Operators - "LT" is big and slow

```
//8-bit less than detector  
//if a is less than b, output is logic one  
module less8(  
    input  [7:0]  a,b,  
    output        z  
);  
    assign z = (a < b) ? 1'b1 : 1'b0;  
endmodule
```

Results from synthesis:

 

Verilog - Operators

Equality Operators

- ▶ logical equality (`==`)
- ▶ logical inequality (`!=`)
- ▶ logical case equality (`===`)
- ▶ logical case inequality (`!==`)

Equality operators return logical 1 if expression is true, else 0

Operands are compared bit by bit

Zero filling is done if operands are of unequal length (**Warning!**)

Logical case inequality allows for checking of x and z values

Checking for X and Z is most definitely non-synthesizable!

Verilog - Operators

Equality Operators (cont.)

```
//let a = 4, b = 3, and...  
//x = 4'b1010, y = 4'b1101,  
//z = 4'b1xxz, m = 4'b1xxz, n = 4'b1xxx
```

```
a == b //evaluates to logical 0  
x != y //evaluates to logical 1  
x == z //evaluates to x  
z === m //evaluates to logical 1  
z === n //evaluates to logical 0  
m !== n //evaluates to logical 1
```

Verilog - Operators

Bitwise Operators

- ▶ negation (\sim), and($\&$), or(\mid), xor(\wedge), xnor(\wedge , \sim)
- ▶ Perform bit-by-bit operation on two operands (except \sim)
- ▶ Mismatched length operands are zero extended
- ▶ x and z treated the same

bitwise AND

	0	1	x
0	0	0	0
1	0	1	x
x	0	x	x

bitwise OR

	0	1	x
0	0	1	x
1	1	1	1
x	x	1	x

bitwise XOR

	0	1	x
0	0	1	x
1	1	0	x
x	x	x	x

bitwise XNOR

	0	1	x
0	1	0	x
1	0	1	x
x	x	x	x

bitwise negation

result

0

1

1

0

x

x

Verilog - Operators

Bitwise Operators (cont.)


- ▶ Logical operators result in logical 1, 0 or x
- ▶ Bitwise operators results in a bit-by-bit value

```
//let x = 4'b1010, y = 4'b0000  
x | y    //bitwise OR, result is 4'b1010  
x || y   //logical OR, result is 1
```

Verilog - Operators

Bitwise operators give bit-by-bit results
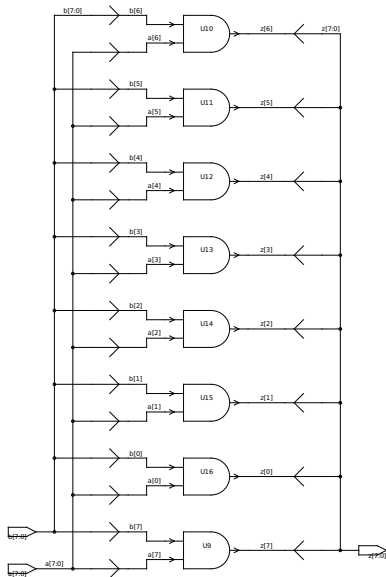
```
//8-bit wide AND
module and8(
    input  [7:0]  a,b,
    output [7:0]  z
);
    assign z = a & b;
endmodule
```



Verilog - Operators

Reduction Operators

- ▶ `and(&)`, `nand(~&)`, `or(|)`, `nor(~|)` `xor(^)`, `xnor(^~,~^)`
- ▶ Operates on only one operand
- ▶ Performs a bitwise operation on all bits of the operand
- ▶ Returns a 1-bit result
- ▶ Works from right to left, bit by bit

```
//let x = 4'b1010
```

```
&x //equivalent to 1 & 0 & 1 & 0. Results in 1'b0
```

```
|x //equivalent to 1 | 0 | 1 | 0. Results in 1'b1
```


```
^x //equivalent to 1 ^ 0 ^ 1 ^ 0. Results in 1'b0
```

A good example of the XOR operator is generation of parity

Verilog - Operators

Reduction Operators
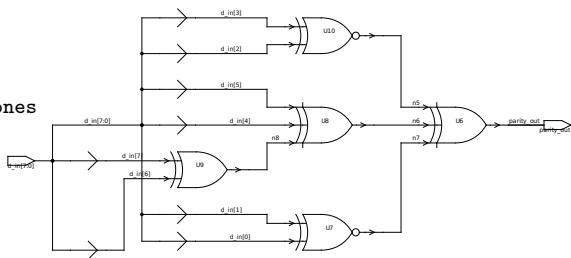
```
//8-bit parity generator  
//output is one if odd # of ones  
module parity8(  
    input  [7:0]  d_in,  
    output        parity_out  
);  
    assign parity_out = ^d_in;  
endmodule
```



Verilog - Operators

Shift Operators

- ▶ right shift (\gg)
- ▶ left shift (\ll)
- ▶ arithmetic right shift (\ggg)
- ▶ arithmetic left shift (\lll)
- ▶ Shift operator shifts a vector operand left or right by a specified number of bits, filling vacant bit positions with zeros.
- ▶ Shifts do not wrap around.
- ▶ Arithmetic shift uses context to determine the fill bits.

```
// let x = 4'b1100
y = x >> 1; // y is 4'b0110
y = x << 1; // y is 4'b1000
y = x << 2; // y is 4'b0000
```

Verilog - Operators

Arithmetic Shift Operators

- ▶ arithmetic right shift (\ggg)
 - ▶ Shift right specified number of bits, fill with value of sign bit if expression is signed, otherwise fill with zero.
- ▶ arithmetic left shift (\lll)
 - ▶ Shift left specified number of bits, filling with zero.

Verilog - Operators

Concatenation Operator {,}

- ▶ Provides a way to append busses or wires to make busses
- ▶ The operands must be sized
- ▶ Expressed as operands in braces separated by commas

```
//let a = 1'b1, b = 2'b00, c = 2'b10, d = 3'b110  
y = {b, c} // y is then 4'b0010  
y = {a, b, c, d, 3'b001} // y is then 11'b10010110001  
y = {a, b[0], c[1]} // y is then 3'b101
```

Verilog - Operators

Replication Operator { { } }

- ▶ Repetitive concatenation of the same number
- ▶ Operands are number of repetitions, and the bus or wire

```
//let a = 1'b1, b = 2'b00, c = 2'b10, d = 3'b110  
y = { 4{a} }           // y = 4'b1111  
y = { 4{a}, 2{b} }      // y = 8'b11110000  
y = { 4{a}, 2{b}, c }   // y = 8'b1111000010
```

Verilog - Operators

Conditional Operator ?:


- ▶ Operates like the C statement
 - ▶ `conditional_expression ? true_expression : false_expression ;`
- ▶ The `conditional_expression` is first evaluated
 - ▶ If the result is true, `true_expression` is evaluated
 - ▶ If the result is false, `false_expression` is evaluated
 - ▶ If the result is `x`:
 - ▶ both true and false expressions are evaluated,...
 - ▶ their results compared bit by bit,...
 - ▶ returns a value of `x` if bits differ, OR...
 - ▶ the value of the bits if they are the same.

This is an ideal way to model a multiplexer or tri-state buffer.

Verilog - Operators

Conditional Operator (cont.)

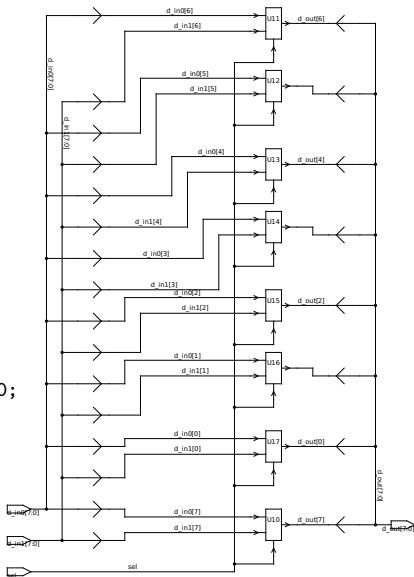
```
//8-bit wide, 2:1 mux
module mux2_1_8wide(
    input sel,
    input  [7:0] d_in1, d_in0,
    output [7:0] d_out
);
    assign d_out = sel ? d_in1 : d_in0;
endmodule
```



Verilog - Operators

Conditional Operator (cont.)
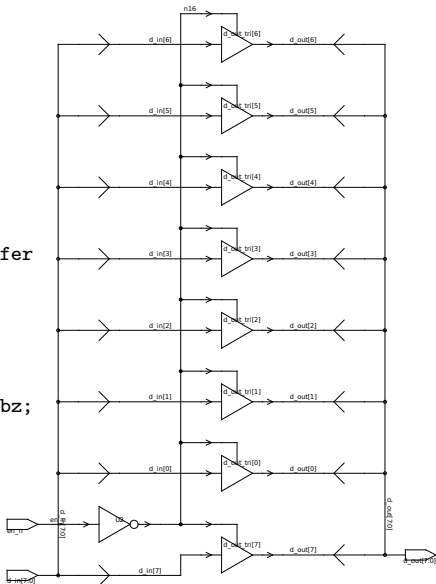
```
//8-bit wide,  
//active-low enabled tri-state buffer  
module ts_buff8(  
    input  [7:0]  d_in,  
    input          en_n,  
    output [7:0]  d_out  
);  
    assign d_out = ~en_n ? d_in : 8'bz;  
endmodule
```



Verilog - Operators

More Lexical Conventions

- ▶ The "assign" statement places a value (a binding) on a wire
- ▶ Also known as a continuous assign
- ▶ A simple way to build combinatorial logic
- ▶ Confusing for complex functions
- ▶ Must be used outside a procedural statement (always)

```
//two input mux, output is z, inputs in1, in2, sel  
assign z = (a | b);  
assign a = in1 & sel;  
assign b = in2 & ~sel;
```

Verilog - Operators

Some More Lexical Conventions

- ▶ The order of execution of the assign statements is unknown
- ▶ We must fake parallel execution... gates operate in parallel
- ▶ The assign statements "fire" when the RHS variables change
- ▶ $RHS = a, b, in1, in2, sel$
- ▶ The values of a, b, and z are updated at the end of the timestep
- ▶ In the next time step if variables changed the next result is posted
- ▶ This repeats until no further changes occur
- ▶ Then..... time advances

```
//two input mux, output is z, inputs in1, in2, sel
assign z = (a | b);
assign a = in1 & sel;
assign b = in2 & ~sel;
```